




ISEL

Departamento de Engenharia
Eletrónica e Telecomunicações
e de Computadores

Licenciatura em Engenharia Informática e de Computadores

 Licenciatura em Engenharia Informática, Redes e Telecomunicações



RELATÓRIO DO 1^o TRABALHO

Circuitos Combinatórios

Trabalho realizado por:

(52718) Alexandre Silva

(52599) Duarte Rodrigues

Turma: 12D

Docente: Pedro Miguens, Sérgio André e Diogo Bastos

Lógica e Sistemas Digitais

2024 / 2025 inverno

Conteúdo

Índice	i
1 Objetivo	1
2 Descrição do Circuito a Projetar	1
3 Desenvolvimento do Projeto	2
3.1 Funções lógicas dos circuitos	2
3.2 Simplificação lógica	3
3.3 Diagrama de blocos	5
4 Resultados e Discussão	8
4.1 Simulação	9
4.2 Teste	10
5 Conclusão	11
Referências	12
A VHDL	13
A.1 alu.vhd	13
A.2 decoder.vhd	20
A.3 mux_2inputs.vhd	22
A.4 flags/flags_main.vhd	23
A.5 flags/odd_parity_checker.vhd	25
A.6 arithmetic_unit/arithmeticunit.vhd	27
A.7 arithmetic_unit/adder_subtractor_4bits.vhd	31
A.8 arithmetic_unit/flags.vhd	35
A.9 arithmetic_unit/full_adder.vhd	37
A.10 arithmetic_unit/half_adder.vhd	40
A.11 arithmetic_unit/inner_arithmetic.vhd	41
A.12 logic_module/logic_module.vhd	44
A.13 logic_module/logical_shift_right.vhd	50

A.14	logic_module/arithmetic_shift_right.vhd	51
A.15	logic_module/logical_shift_left.vhd	52
A.16	logic_module/mux_3inputs.vhd	53
A.17	logic_module/mux_4inputs.vhd	55
A.18	logic_module/nand_gate.vhd	57
B	Atribuição de Pinos	58

1 Objetivo

O objetivo do trabalho é descrever e simular um circuito aritmético e lógico (*ALU - Arithmetic and Logical Unit*) baseado em VHDL estrutural, simulá-lo e implementá-lo na placa de desenvolvimento *DE-10 Lite* da *Intel*.

2 Descrição do Circuito a Projetar

O trabalho tem como objetivo projetar um circuito capaz de realizar as operações aritméticas de adição ($X + Y + CBi$), subtração ($X - Y - CBi$), incrementação ($X - CBi$), decrementação ($X - CBi$) e as operações deslocamento ($X \gg 1$, $X \ll 1$) e a operação lógica de NAND($\overline{X \cdot Y}$)

As entradas são X e Y, operandos de 4 *bits*, CBi um operando de 1 *bit* e a OP, de 3 *bits*, que seleciona a operação a realizar, operação esta que é descodificada a partir do módulo *decoder*.

A saída R é o resultado da operação, estando este, no mesmo domínio dos operandos. Assim, o resultado das operações, (R) gera os indicadores e saídas da *ALU (flags)* Carry/Borrow (CBo), Overflow (OV), Zero (Z), Greater or Equal (GE), Below or Equal (BE) e Parity (P). Na figura 1 encontra-se as operações realizadas pela *ALU*.

OP	Operação	CBo	OV	Z	P	GE	BE
0 0 0	$X + CBi$	X	X	X	X	-	-
0 0 1	$X - CBi$	X	X	X	X	-	-
0 1 0	$X + Y + CBi$	X	X	X	X	-	-
0 1 1	$X - Y - CBi$	X	X	X	X	X	X
1 0 0	$X \gg \gg 1$	X	-	X	X	-	-
1 0 1	$X \gg 1$	X	-	X	X	-	-
1 1 0	$X \ll \ll 1$	X	-	X	X	-	-
1 1 1	$\overline{X \cdot Y}$	-	-	X	X	-	-

Figura 1: Tabela das funções do circuito *ALU*

3 Desenvolvimento do Projeto

3.1 Funções lógicas dos circuitos

As funções do *decoder* foram implementadas através da sua simplificação lógica conforme os mapas de *Karnaugh* utilizados no 3.2, obtendo assim uma tabela de sinais internos correspondentes aos *bits* da entrada OP, Tabela 1.

Na equação (1) podemos obter os mintermos de Z.

$$f(R_3^+, R_2, R_1, R_0^-) = m(0) \quad (1)$$

Na equação (2) podemos obter os mintermos de P.

$$f(R_3^+, R_2, R_1, R_0^-) = \sum m(1, 2, 4, 7, 8, 11, 13, 14) \quad (2)$$


Os *outputs* do bloco de *flags* são obtidos através de um R, resultado da avaliação lógica do *MUX* entre o módulo lógico e o módulo aritmético, um *carry* do LABc3 *module* e um *carry* do *Logic module*, um *overflow* vindo também do LABc *module* e o sinal interno de OPf. Assim, temos que:

- $Ov = (A_3 \cdot B_3 \cdot \overline{R_3}) or (\overline{A_3} \cdot \overline{B_3} \cdot R_3)$
- $CBo = (iCB \cdot \overline{OPf}) or (Cy \cdot OPf)$
- $BE = (iCB) or (Z)$
- $GE = (\overline{R_3} \cdot \overline{Ov}) or (R_3 \cdot Ov)$

Nestes casos, as expressões vêm das entradas ou saídas de diversos componentes da *ALU* (figura 2), sendo assim necessária fazer uma correspondência através dos diversos blocos. Desta forma, conseguimos compreender que por exemplo $A_3 = X_3$, o $B_3 = (Y_3 \cdot OPa) or (0 \cdot \overline{OPa})$ e o CBo do LABc *module* (figura 3) é o iCB usado nas funções devido ao diagrama de blocos do *ALU*.

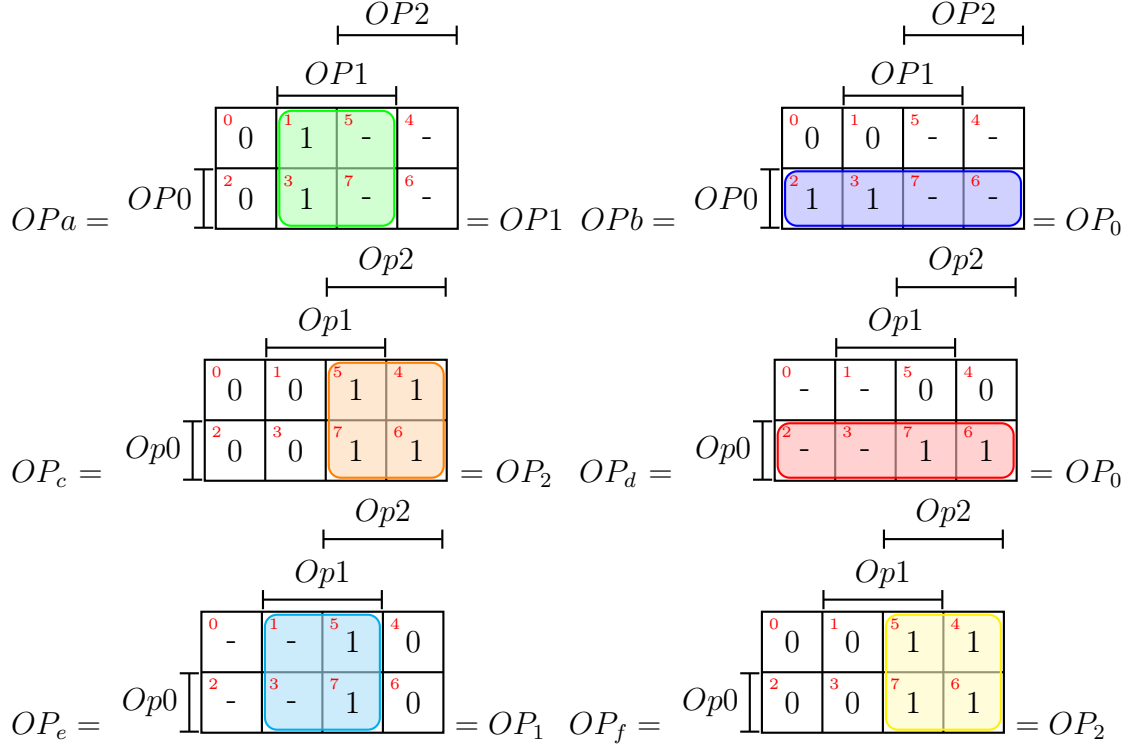3.2 Simplificação lógica

Nos seguintes mapas de *Karnaugh*, podemos constatar que conseguimos obter uma simplificação lógica de cada sinal interno de OP, através de um dos *bits* de OP_{3..0}.



Assim, através destes mapas de *Karnaugh*, temos que:

Sinal Interno	OP _{3..0}
OPa	OP1
OPb	OP0
OPc	OP2
OPd	OP0
OPe	OP1
OPf	OP2

Tabela 1: Simplificações lógicas para o *decoder*.

Desta forma, é possível fazer a correspondência entre os sinais internos de OPa a OPf e os 3 *bits* de entrada de OP.

The diagram shows a 4x4 grid of cells. The cells are labeled with indices in the top-left corner and values in the center. The indices are: (0,0)=0, (0,1)=1, (0,2)=5, (0,3)=4; (1,0)=2, (1,1)=3, (1,2)=7, (1,3)=6; (2,0)=10, (2,1)=11, (2,2)=15, (2,3)=14; (3,0)=8, (3,1)=9, (3,2)=13, (3,3)=12. The cell at (0,1) containing the value 1 is highlighted with a red border. Several regions are indicated by brackets and labels: $R0$ is a vertical bracket on the left side of the first column; $R1$ is a vertical bracket on the left side of the first two rows; $R2$ is a horizontal bracket at the top of the last two columns; $R3$ is a horizontal bracket above the last two rows of the first three columns.

0	1	5	4
2	0	7	6
10	0	15	14
8	0	13	12

4

3.3 Diagrama de blocos

Na Figura 2 encontra-se o Diagrama de blocos ALU.

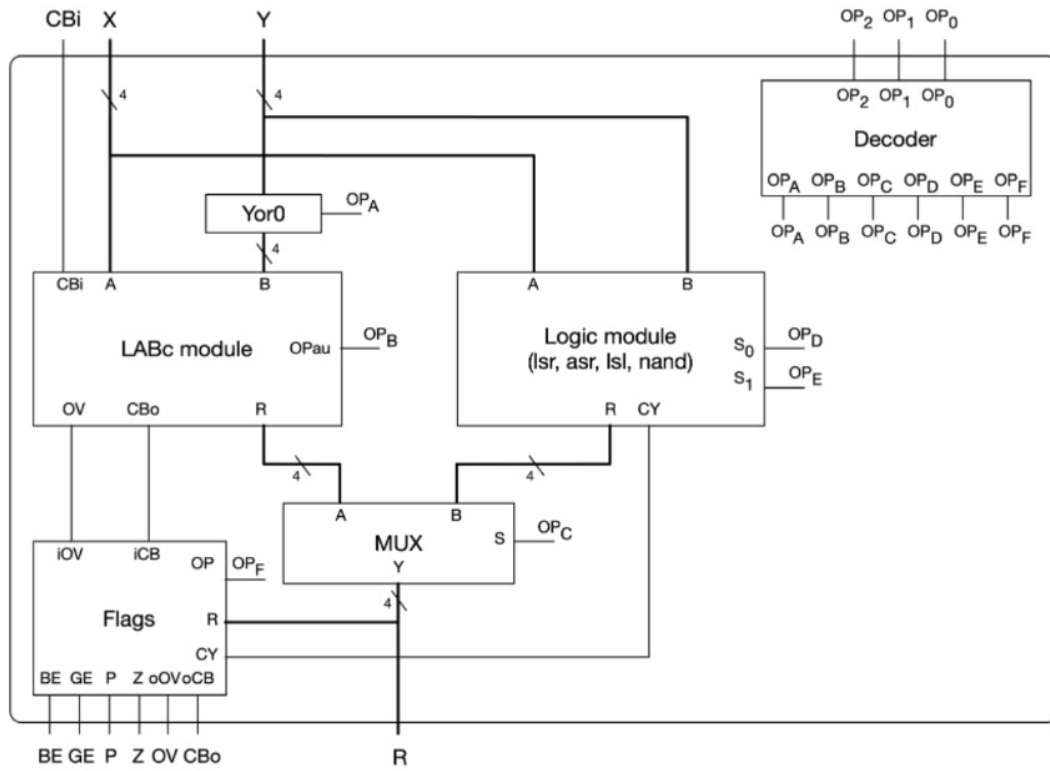


Figura 2: Diagrama de Blocos *ALU*.

Na Figura 3 encontra-se o Diagrama de blocos *LABc module*.

 


Figura 3: Diagrama de Blocos LABc module.

Na Figura 4 encontra-se o Diagrama de blocos. *Logic module*

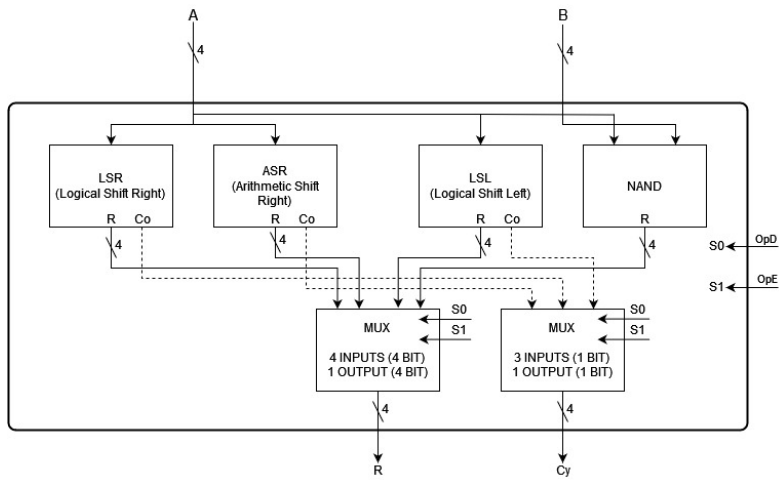


Figura 4: Diagrama de Blocos Logic module.

Na Figura 5 encontra-se o Diagrama de blocos *Flags*.

 


Figura 5: Diagrama de Blocos Flags.

4 Resultados e Discussão

Após a realização de todos os componentes e ligações necessária, o nosso objetivo era verificar se os valores que obtíamos nas simulações estavam de acordo com o esperado.

Para isso, fizemos uso do recurso ao *ModelSim*, onde podemos verificar o comportamento do nosso circuito em relação às nossas entradas (X, Y, CBI e OP) e saídas (R, CBo, OV, Z, P, GE e BE).

O circuito *ALU* foi implementado visando realizar as operações aritméticas (soma, subtração, incremento e decremento), operações de deslocamento (LSL, LSR, ASR) e a operação lógica (NAND), além de gerar os *outputs* apropriados das *flags* e o resultado R.

Durante o processo de simulação pudemos constatar que com diferentes combinações de entradas aplicadas, todos os módulos apresentaram os valores esperados e os sinais intermédios corresponderam sempre aquilo que se pretendia, demonstrando o pleno funcionamento do circuito.

No entanto, nesta fase do trabalho, caso os valores de algum dos módulos demonstrasse valores fora do normal, ou aparecesse como indefinido, através do *ModelSim*, somos capazes de fazer *debug* de verificar os valores intermédios 1 a 1 até encontrar o problema de ligação ou de expressão que estaria a originar o problema.

4.1 Simulação

Realizou-se a simulação do circuito projetado com o objetivo de verificar a funcionalidade deste.

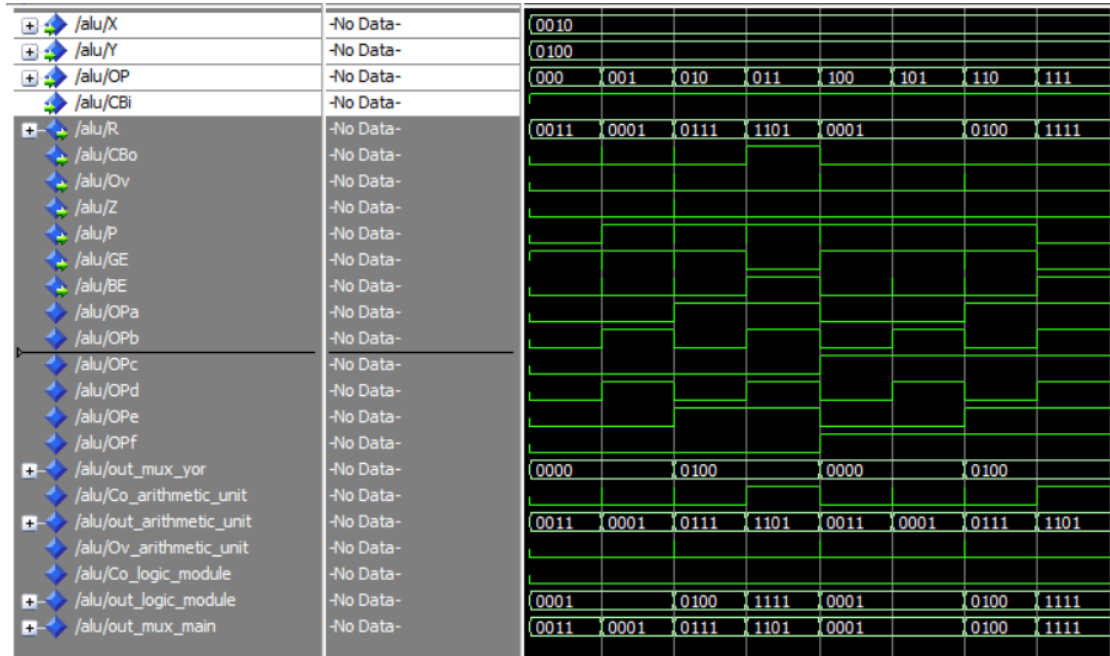


Figura 6: Waves com inputs X=0010, Y=0100, CBi=1.

Na figura 6 está representada a simulação de todas as operações possíveis, feitas com o X=0010, Y=0100 e o CBi=1, sendo assim possível verificar que o circuito está funcional e com os valores corretos.

Além disso, podemos constatar que a simulação continua a dar-nos valores como Ge e Be, mesmo quando a operação a ser realizada não é a de X-Y-CBi, pelo que devemos ter atenção e decidir se os valores fazem sentido de acordo com as operações efetuadas.

4.2 Teste

#	OP	CBI	X(2)	X(N)	X(Z)	Y(2)	Y(N)	Y(Z)	Resultado Teórico								Resultado Experimental									
									R(2)	R(N)	R(Z)	CB0	OV	Z	P	GE	BE	R(2)	R(N)	R(Z)	CB0	OV	Z	P	GE	BE
1	000	0	0000	0	0	1111	15	-1	0000	0	0	0	0	1	0	-	-	0000	0	0	0	0	1	0	-	-
2	000	1	0000	0	0	1111	15	-1	0001	1	+1	0	0	0	1	-	-	0001	1	+1	1	0	0	1	-	-
3	000	1	0111	7	+7	0101	5	+5	1000	8	-8	0	1	0	1	-	-	1000	8	-8	0	1	0	1	-	-
4	000	1	1111	15	-1	1010	10	-6	0000	0	0	1	0	1	0	-	-	0000	0	0	1	0	1	0	-	-
5	001	1	0000	0	+0	1111	15	-1	1111	15	-1	0	0	0	0	-	-	1111	15	-1	0	0	0	0	-	-
6	001	1	0001	1	+1	0101	5	+5	0000	0	0	0	0	1	0	-	-	0000	0	0	0	0	1	0	-	-
7	001	1	1000	8	-8	1010	10	-6	0111	7	+7	1	1	0	1	-	-	0111	7	+7	1	1	0	1	-	-
8	010	0	0001	1	+1	1110	14	-2	1111	15	-1	0	0	0	0	-	-	1111	15	-1	0	0	0	0	-	-
9	010	1	0001	1	+1	1110	14	-2	0000	0	0	1	0	1	0	-	-	0000	0	0	1	0	1	0	-	-
10	010	1	1000	8	-8	1111	15	-1	1000	8	-8	1	1	0	1	-	-	1000	8	-8	1	1	0	1	-	-
11	010	1	0010	2	+2	0101	5	+5	1000	8	-8	0	0	0	1	-	-	1000	8	-8	0	0	0	1	-	-
12	011	0	0011	3	+3	0101	5	+5	1110	14	-2	0	0	0	1	0	1	1110	14	-2	0	0	0	1	0	1
13	011	0	1110	6	+6	1100	12	-4	0010	2	+2	1	0	0	1	1	0	0010	2	+2	1	0	0	1	1	0
14	011	1	0110	6	+6	0110	6	+6	1111	15	-1	1	0	0	0	0	1	1111	15	-1	1	0	0	0	0	1
15	011	1	1000	8	-8	0111	7	+7	0000	0	0	0	1	1	0	0	1	0000	0	0	0	1	1	0	0	1
16	100	1	0001	1	+1	1100	12	-4	0000	0	0	1	-	1	0	-	-	0000	0	0	1	-	1	0	-	-
17	100	0	1101	13	-3	1001	9	-7	0110	6	+6	1	-	0	0	-	-	0110	6	+6	1	-	0	0	-	-
18	101	0	1010	10	-6	1111	15	-1	1101	13	-3	0	-	0	1	-	-	1101	13	-3	0	-	0	1	-	-
19	110	1	1001	9	-7	0110	6	+6	0010	2	+2	1	-	0	1	-	-	0010	2	+2	1	-	0	1	-	-
20	111	1	1111	15	-1	0100	4	+4	1101	11	-5	-	-	0	1	-	-	1101	11	-5	-	-	0	1	-	-
21	001	0	0110	6	+6	0101	5	+5	0110	6	+6	0	0	0	0	-	-	0110	6	+6	0	0	0	0	-	-
22	010	0	0110	6	+6	0101	5	+5	1011	11	-5	0	1	0	1	-	-	1011	11	-5	0	1	0	1	-	-
23	100	1	0110	6	+6	0101	5	+5	0011	3	+3	0	-	0	0	-	-	0011	3	+3	0	-	0	0	-	-
24	111	1	0110	6	+6	0101	5	+5	1011	11	-5	-	-	0	1	-	-	1011	11	-5	-	-	0	1	-	-

Figura 7: Tabela dos testes na Placa DE10-Lite

Nesta fase do trabalho, completamos a tabela com os resultados teóricos, de acordo com os *inputs* ou resultados fornecidos e fizemos a comparação entre os resultados teóricos e os resultados obtidos na placa de testes *DE10-Lite*.

Ao fazermos a comparação, chegamos à conclusão que a placa *DE10-Lite* estava a obter valores em conformidade com o esperado e pudemos concluir que o circuito estava a funcionar em plenas condições. 7

5 Conclusão

O trabalho consistiu em descrever um circuito aritmético e lógico capaz de realizar as operações aritméticas de adição ($X + Y + C_{Bi}$), subtração ($X - Y - C_{Bi}$), incrementação ($X + C_{Bi}$), decrementação ($X - C_{Bi}$) e as operações deslocamento ($X \gg 1$, $X \ll 1$) e a operação lógica de NAND($X \cdot Y$).

Este projeto foi desenvolvido no decorrer da disciplina de Lógica e Sistemas Digitais com o acesso à aplicação *Quartus Prime 20.1 Lite Edition*.

Para tal, foi usado como recurso os mapas de *Karnaugh*, apresentado no ponto 3.2 do relatório, para determinar as funções lógicas que melhor descreviam as expressões necessárias para resolver o problema proposto.

Após a utilização dos mapas de *Karnaugh*, concluímos que não existe simplificação para a expressão lógica da função de paridade ímpar, pelo que a implementamos através do somatório dos mintermos dessa dada função.

A função Z foi implementada através do mintermo (0) como é demonstrado no ponto 3.1 do relatório.

Os *outputs* das flags foram obtidos através do resultado do *MUX* entre os módulos lógico e aritmético e as entradas e saídas destes mesmos módulos, como foi descrito no ponto 3.1.

Além disso foi realizada uma simplificação lógica de forma a obtermos as expressões dos OP usados no *decoder*, no ponto 3.2.

Este circuito foi testado na placa *DE10-Lite* da *Intel* durante a aula laboratorial da disciplina de forma a ter o circuito validado. Os resultados experimentais confirmam o bom funcionamento do circuito, de acordo com os resultados da simulação feita através da *Testbench* utilizada para validar o circuito.

Referências

Referências

- [1] Pedro Miguens Matutino, Sérgio André *Guia de Instalação do Quartus Prime Lite Edition 20.1.1.720*, 2022, ISEL.
- [2] Terasic *DE10-lite User Manual*, 2020, Terasic.

A VHDL

A.1 alu.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This is the main entity of the project, responsible for
-- starting every
-- operation, allowing
entity alu is

    port (
        X      : in std_logic_vector(3 downto 0);
        Y      : in std_logic_vector(3 downto 0);

        OP     : in std_logic_vector(2 downto 0);
        CBi    : in std_logic;

        R      : out std_logic_vector(3 downto 0);
        CBo    : out std_logic;
        Ov     : out std_logic;
        Z      : out std_logic;
        P      : out std_logic;
        GE     : out std_logic;
        BE     : out std_logic
    );

end alu;

architecture behavioral of alu is

    -- Import the arithmetic unit
    component arithmeticunit
```



```

port (
    A    : in std_logic_vector(3 downto 0);
    B    : in std_logic_vector(3 downto 0);

    Ci   : in std_logic;
    Co   : out std_logic;

    OPbit : in std_logic;
    R     : out std_logic_vector(3 downto 0);
    Ov    : out std_logic
);

end component;

-- Import the logic module
component logic_module

port (
    A    : in std_logic_vector(3 downto 0);
    B    : in std_logic_vector(3 downto 0);

    S0   : in std_logic;
    S1   : in std_logic;

    Co   : out std_logic;
    R    : out std_logic_vector(3 downto 0)
);

end component;

-- Import the decoder
component decoder

port (

```

```

    OP2 : in std_logic;
    OP1 : in std_logic;
    OP0 : in std_logic;

    OPa : out std_logic;
    OPb : out std_logic;
    OPc : out std_logic;
    OPd : out std_logic;
    OPe : out std_logic;
    OPf : out std_logic
);

end component;

-- Import the two inputs MUX
component mux_2inputs

port (
    A : in std_logic_vector(3 downto 0);
    B : in std_logic_vector(3 downto 0);

    S : in std_logic;

    R : out std_logic_vector (3 downto 0)
);

end component;

-- Import the two inputs MUX
component flags_main

port (
    Ov      : in std_logic;
    CBi_au  : in std_logic;
    CBi_lm  : in std_logic;

```

```

    R_mux    : in std_logic_vector(3 downto 0);
    OPf      : in std_logic;

    CBo      : out std_logic;
    Ov_out   : out std_logic;
    BE       : out std_logic;
    GE       : out std_logic;
    P        : out std_logic;
    Zs       : out std_logic
  );

end component;

-- Defines all the operation signals to be used
signal OPa : std_logic;
signal OPb : std_logic;
signal OPc : std_logic;
signal OPd : std_logic;
signal OPe : std_logic;
signal OPf : std_logic;

-- Defines all the output signals
signal out_mux_yor      : std_logic_vector(3 downto 0);
signal Co_arithmetic_unit : std_logic;
signal out_arithmetic_unit : std_logic_vector(3 downto 0);
signal Ov_arithmetic_unit : std_logic;
signal Co_logic_module   : std_logic;
signal out_logic_module  : std_logic_vector(3 downto 0);
signal out_mux_main      : std_logic_vector(3 downto 0);

begin

-- Instantiate the main decoder, to translate the operation
  bits to the A-F signals
instance_decoder : decoder

```

```

port map (
    OP2 => OP(2),
    OP1 => OP(1),
    OP0 => OP(0),

    OPa => OPa,
    OPb => OPb,
    OPc => OPc,
    OPd => OPd,
    OPe => OPe,
    OPf => OPf
);

-- Instantiates the 2 inputs MUX that will serve as a YOR
instance_yor : mux_2inputs

port map (
    A => "0000",
    B => Y,
    S => OPa,

    R => out_mux_yor
);

-- Instantiates the arithmetic unit to perform math
operations
instance_arithmetic_unit : arithmeticunit

port map (
    A => X,
    B => out_mux_yor,

```

```

    Ci => CBi,
    Co => Co_arithmetic_unit,

    OPbit => OPb,
    R      => out_arithmetic_unit,
    Ov     => Ov_arithmetic_unit
);

-- Instantiates the logic module for any relational or
-- logical operations
instance_logic_module : logic_module

port map (
    A => X,
    B => Y,

    S0 => OPd,
    S1 => OPe,

    Co => Co_logic_module,
    R  => out_logic_module
);

-- Instantiates the MUX used to connect the logic module
-- and arithmetic unit
instance_mux : mux_2inputs

port map (
    A => out_arithmetic_unit,
    B => out_logic_module,
    S => OPc,

    R => out_mux_main

```

```

);

-- Instantiates the flags module
instance_flags : flags_main

port map (
    Ov      => Ov_arithmetic_unit ,
    CBi_au  => Co_arithmetic_unit ,
    CBi_lm  => Co_logic_module ,
    R_mux   => out_mux_main ,
    OPf     => OPf ,

    CBo     => CBo ,
    Ov_out  => Ov ,
    BE      => BE ,
    GE      => GE ,
    P       => P ,
    Z_out   => Z
);

R <= out_mux_main;

end behavioral;

```

A.2 decoder.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting as a decoder,
-- allowing us to select
-- different operations on the ALU
entity decoder is

    port (
        OP2 : in std_logic;
        OP1 : in std_logic;
        OP0 : in std_logic;

        OPa : out std_logic;
        OPb : out std_logic;
        OPc : out std_logic;
        OPd : out std_logic;
        OPe : out std_logic;
        OPf : out std_logic
    );

end decoder;

architecture structural of decoder is
begin

    OPa <= OP1;
    OPb <= OP0;
    OPc <= OP2;
    OPd <= OP0;
    OPe <= OP1;
    OPf <= OP2;
```

```
end structural;
```


A.3 mux_2inputs.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting like a MUX, and
-- giving the output based
-- on the selected inputs
entity mux_2inputs is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        S : in std_logic;

        R : out std_logic_vector(3 downto 0)
    );

end mux_2inputs;

-- Implements the logic of a MUX with two inputs and one
-- selector
architecture structural of mux_2inputs is

    signal S4bit : std_logic_vector(3 downto 0);

begin

    S4bit <= S & S & S & S;
    R <= (A and not(S4bit)) or (B and S4bit);

end structural;
```

A.4 flags/flags_main.vhd

```
library ieee;
use ieee.std_logic_1164.all;

entity flags_main is

    port (
        Ov      : in std_logic;
        CBi_au   : in std_logic;
        CBi_lm   : in std_logic;
        R_mux    : in std_logic_vector(3 downto 0);
        OPf      : in std_logic;

        CBo      : out std_logic;
        Ov_out    : out std_logic;
        BE       : out std_logic;
        GE       : out std_logic;
        P        : out std_logic;
        Z_out    : out std_logic
    );

end flags_main;

architecture behavioral of flags_main is

    -- Import the odd_P_checker
    component odd_parity_checker

        port (
            I0 : in std_logic;
            I1 : in std_logic;
            I2 : in std_logic;
            I3 : in std_logic;
```

```

        P : out std_logic;
        Z : out std_logic
    );

end component;

signal Z_signal : std_logic;

begin

    -- Instantiation of the odd_parity_checker
    instance_odd_parity_checker : odd_parity_checker

    port map (
        I0 => R_mux(0),
        I1 => R_mux(1),
        I2 => R_mux(2),
        I3 => R_mux(3),

        P => P,
        Z => Z_signal
    );

    Z_out    <= Z_signal;
    Ov_out   <= Ov;
    BE       <= CBi_au or Z_signal;
    GE       <= not (R_mux(3) or Ov) or (Ov and R_mux(3));
    CBo      <= (CBi_lm and OPf) or (CBi_au and not OPf);

end behavioral;

```

A.5 flags/odd_parity_checker.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- Declaration of odd_parity_checker with inputs between I0
-- and I3 and outputs P and Z
entity odd_parity_checker is
  port
  (
    I0 : in std_logic;
    I1 : in std_logic;
    I2 : in std_logic;
    I3 : in std_logic;

    P : out std_logic;
    Z : out std_logic
  );
end odd_parity_checker;

architecture structural of odd_parity_checker is

  -- Declaration of the minterm signals where the output P is
  -- on
  signal minterm_1   : std_logic;
  signal minterm_2   : std_logic;
  signal minterm_4   : std_logic;
  signal minterm_7   : std_logic;
  signal minterm_8   : std_logic;
  signal minterm_11  : std_logic;
  signal minterm_13  : std_logic;
  signal minterm_14  : std_logic;
```

```

begin

    -- Odd input minterms
    minterm_1  <= (not (I0 or I1 or I2) and I3);
    minterm_2  <= (not (I0 or I1 or I3) and I2);
    minterm_4  <= (not (I0 or I2 or I3) and I1);
    minterm_7  <= (not I0 and (I1 and I2 and I3));
    minterm_8  <= (not (I1 or I2 or I3) and I0);
    minterm_11 <= (not I1 and (I0 and I2 and I3));
    minterm_13 <= (not I2 and (I0 and I1 and I3));
    minterm_14 <= (not I3 and (I0 and I1 and I2));

    -- P is on when either of the odd minterms is on
    -- Z is on when none of the inputs are on
    P <= (minterm_1 or minterm_2 or minterm_4 or minterm_7 or
          minterm_8 or minterm_11 or minterm_13 or minterm_14);
    Z <= (not (I0 or I1 or I2 or I3));

end structural;

```

A.6 arithmetic_unit/arithmeticunit.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for taking in two 4-bit
-- integers and adding
-- them together, allowing for a carry in, and a carry out
-- and an operation
-- variable to decide whether to subtract or add
entity arithmeticunit is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        Ci : in std_logic;
        Co : out std_logic;

        OPbit : in std_logic;
        R      : out std_logic_vector(3 downto 0);
        Ov      : out std_logic
    );

end arithmeticunit;

architecture behavioral of arithmeticunit is

    -- Import the flagging circuit
    component flags

        port (
            A : in std_logic;
            B : in std_logic;
```

```

    R : in std_logic;

    Ci : in std_logic;
    Co : out std_logic;

    Ov : out std_logic
);

end component;

-- Import the inner arithmetic circuit
component inner_arithmetic

port (
    A : in std_logic_vector;
    B : in std_logic_vector;

    Ci      : in std_logic;
    OPbit   : in std_logic;

    R        : out std_logic_vector(3 downto 0);
    Co       : out std_logic;
    B3_output : out std_logic
);

end component;

-- Declares an intermediate "out_inner_arithmetic" signal
-- so that we can
-- read its bits afterwards, the carry and a xor'd b3
-- signal with the
-- operation bit, use inside the flags
signal out_inner_arithmetic : std_logic_vector(3 downto 0);

```

```

signal Ciner_arithmetic : std_logic;
signal B3_xor : std_logic;

begin

    -- Instantiate the inner arithmetic, whose parameters are
    -- mostly the same
    -- as the ones we have in the AU, due to it just being a
    -- layer of abstraction
    instance_inner_arithmetic : inner_arithmetic

    port map (
        A => A,
        B => B,

        Ci      => Ci,
        OPbit    => OPbit,

        R        => out_inner_arithmetic,
        Co        => Ciner_arithmetic,
        B3_output => B3_xor
    );

    -- Instantiate the flags unit
    instance_flags : flags

    port map (
        A => A(3),
        B => B3_xor,
        R => out_inner_arithmetic(3),

        Ci => Ciner_arithmetic,
        Co => Co,

```



```
        Ov => Ov
    );

    R <= out_inner_arithmetic;

end behavioral;
```

A.7 arithmetic_unit/adder_subtractor_4bits.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for taking in two 4-bit
-- integers and adding
-- them together, allowing for a carry in, and a carry out
-- and an operation
-- variable to decide whether to subtract or add
entity adder_subtractor_4bits is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        Ci : in std_logic;
        Co : out std_logic;

        R : out std_logic_vector(3 downto 0)
    );

end adder_subtractor_4bits;

architecture behavioral of adder_subtractor_4bits is

    -- Imports the full adder from the specification in the
    -- full_adder entity
    component full_adder

        port (
            A : in std_logic;
            B : in std_logic;
```

```

    Ci : in std_logic;
    Co : out std_logic;

    R : out std_logic
);

end component;

-- Declares the output and carry variables for the 4 full
  adders
signal out_full_adder_1 : std_logic;
signal out_full_adder_2 : std_logic;
signal out_full_adder_3 : std_logic;
signal out_full_adder_4 : std_logic;

signal carry_full_adder_1 : std_logic;
signal carry_full_adder_2 : std_logic;
signal carry_full_adder_3 : std_logic;
signal carry_full_adder_4 : std_logic;

begin

-- Instantiates a full adder with all the default values
instance_full_adder_1 : full_adder

port map (
    A => A(0),
    B => B(0),

    Ci => Ci,
    Co => carry_full_adder_1,

    R => out_full_adder_1
);

```

```

-- Instantiates three more full adders with the previous
  carries as inputs
-- and with incremental bit placements for the A and B
  inputs
instance_full_adder_2 : full_adder

port map (
  A => A(1),
  B => B(1),

  Ci => carry_full_adder_1,
  Co => carry_full_adder_2,

  R => out_full_adder_2
);

instance_full_adder_3 : full_adder

port map (
  A => A(2),
  B => B(2),

  Ci => carry_full_adder_2,
  Co => carry_full_adder_3,

  R => out_full_adder_3
);

instance_full_adder_4 : full_adder

port map (

```

```

    A => A(3),
    B => B(3),

    Ci => carry_full_adder_3,
    Co => carry_full_adder_4,

    R => out_full_adder_4
);

-- Defines the adder/subtractor's carry out as the last
-- full adder's carry
Co <= carry_full_adder_4;

-- Sets the R bits in order
R(0) <= out_full_adder_1;
R(1) <= out_full_adder_2;
R(2) <= out_full_adder_3;
R(3) <= out_full_adder_4;

end behavioral;

```

A.8 arithmetic_unit/flags.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is simply responsible for checking whether
-- there's overflow and
-- a carry out (Ov for unsigned integers and carry out for
-- signed ints)
-- and outputting it for later use
entity flags is

    port (

        -- A and B are the most significant bits for both numbers
        -- (see diagram)
        -- If these bits are 0, it's a positive integer.
        -- If they're 1, it's a negative integer.
        A : in std_logic;
        B : in std_logic;
        R : in std_logic;  -- R is the most significant bit for
                           -- the result

        Ci : in std_logic;
        Co : out std_logic;

        Ov : out std_logic
    );

end flags;

architecture behavioral of flags is
begin
```

```
Co <= Ci;  
Ov <= ((A and B and not R) or (not A and not B and R));  
  
end behavioral;
```

A.9 arithmetic_unit/full_adder.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting as a full adder,
-- using two half-adders
-- in succession to account for first bit carries
entity full_adder is

    port (
        A : in std_logic;
        B : in std_logic;

        Ci : in std_logic;
        Co : out std_logic;

        R : out std_logic
    );

end full_adder;

architecture behavioral of full_adder is

    -- Imports the half adder from the specification in the
    -- half_adder entity
    component half_adder

        port (
            A : in std_logic;
            B : in std_logic;

            R : out std_logic;
```



```

        Co  : out std_logic
    );

end component;

-- Initialises the R carriers for the half-adders
signal out_half_adder_1 : std_logic;
signal out_half_adder_2 : std_logic;

signal carry_half_adder_1 : std_logic;
signal carry_half_adder_2 : std_logic;

begin

    -- Instantiate the first half adder with the full adder's A
    -- and B
    instance_half_adder_1 : half_adder

    port map (
        A => A,
        B => B,

        R  => out_half_adder_1,
        Co => carry_half_adder_1
    );

    -- Instantiate the second half adder with the first half
    -- adder's R and
    -- carry, to account for the bit carry
    instance_half_adder_2: half_adder

    port map (
        A => out_half_adder_1,

```

```
B => Ci ,

R  => out_half_adder_2 ,
Co => carry_half_adder_2
);

R  <= out_half_adder_2;
Co <= (carry_half_adder_1 or carry_half_adder_2);

end behavioral;
```

A.10 arithmetic_unit/half_adder.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting as a half adder,
-- simply XOR'ing two
-- to sum them returning their value and carry.
entity half_adder is

    port (
        A : in std_logic;
        B : in std_logic;

        R  : out std_logic;
        Co : out std_logic
    );

end half_adder;

architecture structural of half_adder is
begin

    R    <= A xor B;
    Co   <= A and B;

end structural;
```

A.11 arithmetic_unit/inner_arithmetic.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for handling the inner
-- arithmetic logic excluding
-- the circuit flags. Whether the calculation is a
-- subtraction or addition is also
-- handled here
entity inner_arithmetic is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        Ci      : in std_logic;
        OPbit   : in std_logic;

        R        : out std_logic_vector(3 downto 0);
        Co        : out std_logic;
        B3_output : out std_logic
    );

end inner_arithmetic;

architecture behavioral of inner_arithmetic is

    -- Import the 4 bit adder/subtractor
    component adder_subtractor_4bits

        port (
            A : in std_logic_vector(3 downto 0);
            B : in std_logic_vector(3 downto 0);
```

```

    Ci : in std_logic;
    Co : out std_logic;

    R : out std_logic_vector(3 downto 0)
);

end component;

-- Declares a temporary variable to store the adder output
-- for later
signal carry_adder_subtractor_4bits : std_logic;
signal carry_adder_subtractor_4bits2 : std_logic;
signal b_xor : std_logic_vector(3 downto 0);

begin

    b_xor(0) <= B(0) xor OPbit;
    b_xor(1) <= B(1) xor OPbit;
    b_xor(2) <= B(2) xor OPbit;
    b_xor(3) <= B(3) xor OPbit;

    -- Instantiates the adder/subtractor setting its R as the
    -- inner
    -- arithmetic R, and outputting the carry to XOR it with
    -- the operation bit
    instance_adder_subtractor_4bits : adder_subtractor_4bits

    port map (
        A => A,
        B => b_xor,

        Ci => carry_adder_subtractor_4bits2,
        Co => carry_adder_subtractor_4bits,

```

```

        R => R
    );

    carry_adder_subtractor_4bits2 <= Ci xor OPbit;
    Co          <= carry_adder_subtractor_4bits xor OPbit;
    B3_output <= b_xor(3);

end behavioral;

```

A.12 logic_module/logic_module.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for the operation logic
  functions
entity logic_module is

    port (
        A      : in std_logic_vector(3 downto 0);
        B      : in std_logic_vector(3 downto 0);

        S0 : in std_logic;
        S1 : in std_logic;

        Co      : out std_logic;
        R      : out std_logic_vector(3 downto 0)
    );

end logic_module;

architecture behavioral of logic_module is

    -- Import of the logical_shift_right circuit
    component logical_shift_right

        port (
            input : in std_logic_vector(3 downto 0);

            R      : out std_logic_vector(3 downto 0);
            Co      : out std_logic
        );
```

```

end component;

-- Import of the arithmetic_shift_right circuit
component arithmetic_shift_right

    port (
        input : in std_logic_vector(3 downto 0);

        R      : out std_logic_vector(3 downto 0);
        Co     : out std_logic
    );

end component;

-- Import of the logical_shift_left circuit
component logical_shift_left

    port (
        input : in std_logic_vector(3 downto 0);

        R      : out std_logic_vector(3 downto 0);
        Co     : out std_logic
    );

end component;

-- Import of the nand_gate circuit
component nand_gate

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        R : out std_logic_vector(3 downto 0)
    );

```



```

end component;

-- Import of the mux_4inputs circuit
component mux_4inputs

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        C : in std_logic_vector(3 downto 0);
        D : in std_logic_vector(3 downto 0);

        S0 : in std_logic;
        S1 : in std_logic;

        R  : out std_logic_vector(3 downto 0)
    );

end component;

-- Import of the mux_3inputs circuit
component mux_3inputs

    port (
        A : in std_logic;
        B : in std_logic;
        C : in std_logic;

        S0 : in std_logic;
        S1 : in std_logic;

        R  : out std_logic
    );

end component;

```

```

-- Signal of logical_shift_right
signal out_logical_shift_right : std_logic_vector(3 downto
    0);
signal carry_logical_shift_right : std_logic;

-- Signal of arithmetic_shift_right
signal out_arithmetic_shift_right : std_logic_vector(3
    downto 0);
signal carry_arithmetic_shift_right : std_logic;

-- Signal of logical_shift_left
signal out_logical_shift_left : std_logic_vector(3 downto
    0);
signal carry_logical_shift_left : std_logic;

-- Signal of nand_gate
signal out_nand_gate : std_logic_vector(3 downto 0);

-- Signals for the mux of 4 inputs for the carries
signal out_mux_3inputs_carries : std_logic;

begin

-- Instantiation of the logical_shift_right
instance_logical_shift_right : logical_shift_right

    port map (
        input => A,

        R      => out_logical_shift_right,
        Co     => carry_logical_shift_right
    );

```

```

-- Instantiation of the arithmetic_shift_right
instance_arithmetic_shift_right : arithmetic_shift_right

port map (
    input => A,

    R      => out_arithmetic_shift_right,
    Co     => carry_arithmetic_shift_right
);

-- Instantiation of the logical_shift_left
instance_logical_shift_left : logical_shift_left

port map (
    input => A,

    R      => out_logical_shift_left,
    Co     => carry_logical_shift_left
);

-- Instantiation of the nand_gate
instance_logical_nand_gate : nand_gate

port map (
    A => A,
    B => B,

    R => out_nand_gate
);

```

```

-- Instantiation of the mux_4inputs
instance_mux_4inputs : mux_4inputs

port map (
    A => out_logical_shift_right,
    B => out_arithmetic_shift_right,
    C => out_logical_shift_left,
    D => out_nand_gate,

    S0 => S0,
    S1 => S1,

    R  => R
);

-- Instantiation of the mux_3inputs for the carries,
  representing
-- the carry bits in 3bit forms
instance_mux_3inputs : mux_3inputs

port map (
    A => carry_logical_shift_right,
    B => carry_arithmetic_shift_right,
    C => carry_logical_shift_left,

    S0 => S0,
    S1 => S1,

    R  => out_mux_3inputs_carries
);

-- Extract the first bit from the R
Co <= out_mux_3inputs_carries;

end behavioral;

```

A.13 logic_module/logical_shift_right.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsibly for shifting an input to the
-- right, effectively
-- dividing the input by two

entity logical_shift_right is

    port (
        input : in std_logic_vector(3 downto 0);

        R      : out std_logic_vector(3 downto 0);
        Co     : out std_logic
    );

end logical_shift_right;

architecture structural of logical_shift_right is
begin

    R(0) <= input(1);
    R(1) <= input(2);
    R(2) <= input(3);
    R(3) <= '0';

    Co   <= input(0);

end structural;
```

A.14 logic_module/arithmetic_shift_right.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for shifting a number to the
-- right, effectively
-- dividing the number by two, while still putting the most
-- significant bit on the leftmost digit
entity arithmetic_shift_right is

    port (
        input : in std_logic_vector(3 downto 0);

        Co    : out std_logic;
        R      : out std_logic_vector(3 downto 0)
    );

end arithmetic_shift_right;

architecture structural of arithmetic_shift_right is
begin

    R(0) <= input(1);
    R(1) <= input(2);
    R(2) <= input(3);
    R(3) <= input(3);

    Co    <= input(0);

end structural;
```

A.15 logic_module/logical_shift_left.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for shifting a number to the
-- left, effectively
-- multiplying the number by two, while adding a '0' to the
-- less significant bit
entity logical_shift_left is

    port (
        input      : in std_logic_vector(3 downto 0);

        Co         : out std_logic;
        R          : out std_logic_vector(3 downto 0)
    );

end logical_shift_left;

architecture structural of logical_shift_left is
begin

    R(0) <= '0';
    R(1) <= input(0);
    R(2) <= input(1);
    R(3) <= input(2);

    Co   <= input(3);

end structural;
```

A.16 logic_module/mux_3inputs.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting like a MUX, and
-- giving the output based
-- on the selected inputs
entity mux_3inputs is

    port (
        A : in std_logic;
        B : in std_logic;
        C : in std_logic;

        S0 : in std_logic;
        S1 : in std_logic;

        R : out std_logic
    );

end mux_3inputs;

-- Implements the logic of a MUX with three inputs and two Ss
architecture structural of mux_3inputs is

    -- For readability, separate every MUX's path into
    -- intermediate checks
    -- based on the MUX R
    signal path_A : std_logic;
    signal path_B : std_logic;
    signal path_C : std_logic;

begin
```



```
path_A <= A and (not S0) and (not S1);  
path_B <= B and S0 and (not S1);  
path_C <= C and (not S0) and S1;  
  
R <= path_A or path_B or path_C;  
  
end structural;
```

A.17 logic_module/mux_4inputs.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for acting like a MUX, and
-- giving the output based
-- on the selected inputs
entity mux_4inputs is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);
        C : in std_logic_vector(3 downto 0);
        D : in std_logic_vector(3 downto 0);

        S0 : in std_logic;
        S1 : in std_logic;

        R : out std_logic_vector (3 downto 0)
    );

end mux_4inputs;

-- Implements the logic of a MUX with four inputs and two Ss
architecture structural of mux_4inputs is

    -- For readability, separate every MUX's path into
    -- intermediate checks
    -- based on the MUX R
    signal path_A : std_logic_vector(3 downto 0);
    signal path_B : std_logic_vector(3 downto 0);
    signal path_C : std_logic_vector(3 downto 0);
    signal path_D : std_logic_vector(3 downto 0);
```

```

-- Signals for the operation bit 4bit conversion
signal S04bit : std_logic_vector(3 downto 0);
signal S14bit : std_logic_vector(3 downto 0);

begin

-- Assigns every path to its logical expression (the one
  that will conduct
-- its R signal)
S04bit <= S0 & S0 & S0 & S0;
S14bit <= S1 & S1 & S1 & S1;

path_A <= A and (not S04bit) and (not S14bit);
path_B <= B and S04bit and (not S14bit);
path_C <= C and (not S04bit) and S14bit;
path_D <= D and S04bit and S14bit;

R <= path_A or path_B or path_C or path_D;

end structural;

```

A.18 logic_module/nand_gate.vhd

```
library ieee;
use ieee.std_logic_1164.all;

-- This entity is responsible for performing a NAND operation
-- between two inputs
entity nand_gate is

    port (
        A : in std_logic_vector(3 downto 0);
        B : in std_logic_vector(3 downto 0);

        R : out std_logic_vector(3 downto 0)
    );

end nand_gate;

architecture structural of nand_gate is
begin

    R <= not (A and B);

end structural;
```

B Atribuição de Pinos

Entradas	Pino
X(0)	C10
X(1)	C11
X(2)	D12
X(3)	C12
Y(0)	A12
Y(1)	B12
Y(2)	A13
Y(3)	A14
OP(0)	B14
OP(1)	F15
OP(2)	B8
CBi	A7
Saídas	Pino
BE	B11
GE	A11
OV	C13
CBo	D13
P	D14
Z	E14
R(0)	A8
R(1)	A9
R(2)	A10
R(3)	B10

Tabela 2: Atribuição de pinos para a o circuito *ALU* [2]